

Assignment 7

K GANESH REDDY

January 10, 2021

1 Boolean Expression

$$a = D'.B'.(C.A' + C'A)$$

2 Nand Gates for the above expression

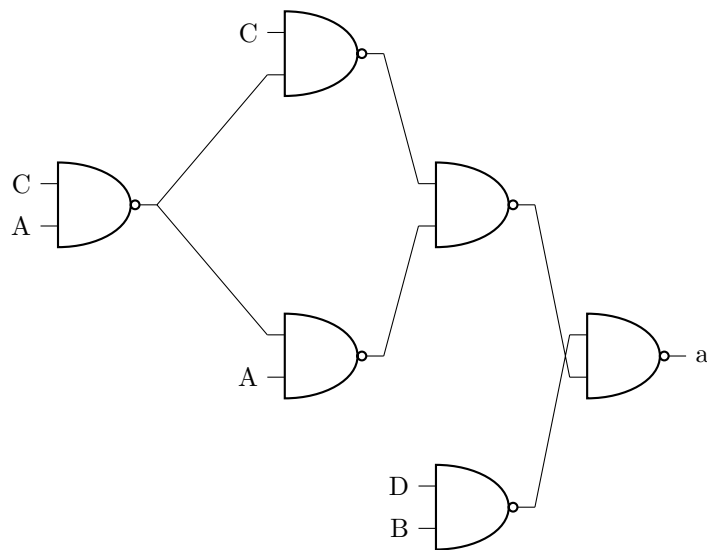


Figure 1: Logic Gate for NAND logic

$$a = D'.B'.(C.A' + C'A) \quad (1)$$