

Assignment 7

K GANESH REDDY

January 8, 2021

1 question

The expression $\sim (p \leftrightarrow q)$ is equivalent to:

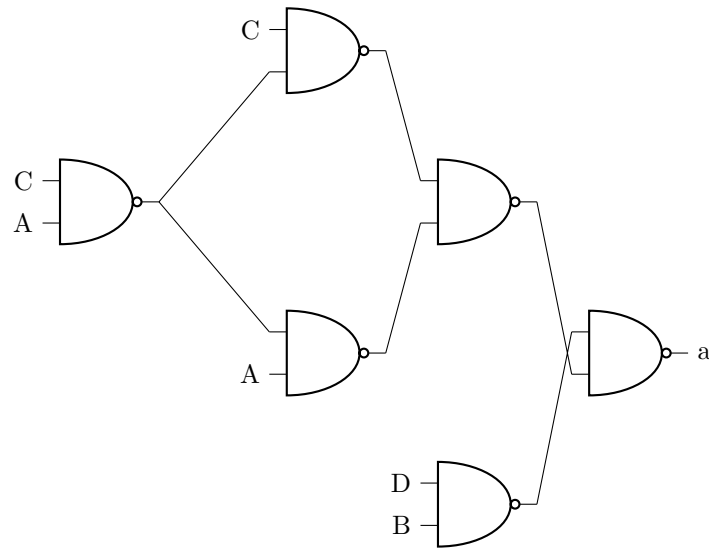


Figure 1: Logic Gate for NAND logic

$$a = D'.B'.(C.A' + C'A) \quad (1)$$