

Digital Logic Design Assignment 6

k ganesh reddy

January 8, 2021

1 Boolean Equation

$$a = D' B'(C A' + C'A)$$

2 Logic Diagram

